

2013 HIGHER SCHOOL CERTIFICATE EXAMINATION

Industrial Technology Electronics Technologies

General Instructions

- Reading time 5 minutes
- Working time $1\frac{1}{2}$ hours
- Write using black or blue pen Black pen is preferred
- Draw diagrams using pencil
- Board-approved calculators may be used
- Write your Centre Number and Student Number at the top of page 9

Total marks - 40

Section I Pages 2–5

10 marks

- Attempt Questions 1–10
- Allow about 20 minutes for this section

Section II Pages 9–12

15 marks

- Attempt Questions 11–15
- Allow about 35 minutes for this section

Section III Page 13

15 marks


- Attempt Question 16
- Allow about 35 minutes for this section

Section I


10 marks Attempt Questions 1–10 Allow about 20 minutes for this section

Use the multiple-choice answer sheet for Questions 1–10.

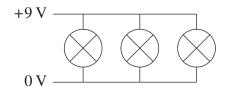
- 1 Electric current is the flow of which particles?
 - (A) Atoms
 - (B) Electrons
 - (C) Neutrons
 - (D) Protons
- Which statement is true for the circuit shown?



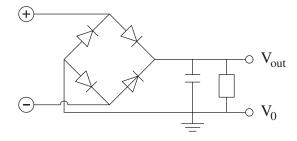- (A) The voltage across each component is the same.
- (B) The current across each component is the same.
- (C) The voltage across each component is different.
- (D) The capacitance across each component is different.
- 3 What is the function of the circuit shown?



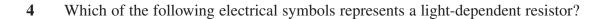- (A) To convert AC voltage to DC voltage
- (B) To prevent voltage surges in a circuit
- (C) To reduce voltage output from a circuit
- (D) To increase voltage output from a circuit











5 What is the resistance in an electric kettle rated at 5 amps on a domestic 240V supply?

- (A) 5Ω
- (B) 24Ω
- (C) 48Ω
- (D) 1200Ω

6 What is the main advantage of a relay switch?

- (A) It can be manually or electromagnetically operated.
- (B) The electromagnetic switch contacts never get dirty.
- (C) Low voltage input sources allow larger voltage outputs.
- (D) High voltage inputs are reduced across the electromagnetic switch.

A teacher has planned a class project where each student is required to make a simple LED torch. The table shows the materials required and the costs.

Quantity required per torch	Description	Supply Cost
1	PCB board	\$1.25 each
1	12V battery	\$3.19 each
1	12V battery holder	\$0.90 each
3	Super bright white LED	\$1.10 each
1	680 ohm resistor	\$0.05 each
1	Slide switch – SPST	\$1.45 each

What is the total cost of supplying the materials for a class of 24 students?

- (A) \$10.14
- (B) \$190.56
- (C) \$243.36
- (D) \$486.72

8 The incomplete truth table for an AND gate is shown.

Inp	Output	
A	В	Q
0	0	
0	1	
1	0	
1	1	

Which of the following shows the correct outputs in column Q?


- 9 In a circuit, a thermistor is a type of resistor designed to
 - (A) dissipate heat by vibration.
 - (B) burn out if power is excessive.
 - (C) prevent heat expansion in a circuit.
 - (D) change resistance with changes in heat.
- 10 What is an operational amplifier (op amp)?
 - (A) A high gain linear device for use in digital circuits
 - (B) A high gain linear device for use in analog circuits
 - (C) A high gain non-linear device for use in digital circuits
 - (D) A high gain non-linear device for use in analog circuits

Industrial Technology Electronics Technologies				C	Centre	Nur	mber
Section II							
15 marks Attempt Questions 11–15 Allow about 35 minutes for this section				St	udent	t Nur	nber
Answer the questions in the spaces provided. These length of response.	spaces p	rovide	e guid	ance fo	r the	expe	ected
Question 11 (2 marks)							
List TWO common faults that could be identified be circuit that is not working.	oy a vist	ial ins	spection	on of a	PCB	}	2
	••••••	•••••	•••••		• • • • • • • • • • • • • • • • • • • •	•	
		••••••	•••••		• • • • • • • • • • • • • • • • • • • •		

Please turn over

2431 - 9 -

Question 12 (3 marks)

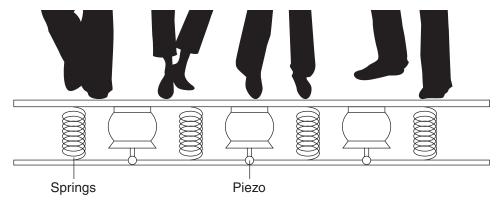


The diagram shows the sprung floor of a dance club that uses piezo devices to create lighting effects as people dance.	3
Explain how the piezo devices are used to achieve this effect.	
Question 13 (3 marks)	
Describe the operation of a stepped motor and provide an example of its application.	3

Question 14 (3 marks)

Calculate the readings on the voltmeter and ammeter in the circuit below. Show your working.

3

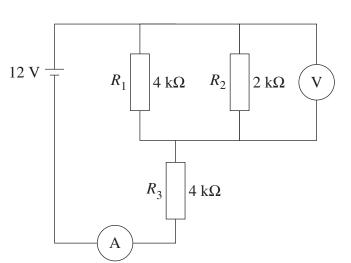


•••••	•••••	• • • • • • • • • • • • • • • • • • • •	•••••	• • • • • • • • • • • • • • • • • • • •	• • • • • • • • • • • • • • • • • • • •	• • • • • • • • • • • • • • • • • • • •	• • • • • • • • • • • • • • • • • • • •	•••••	• • • • • • • • • • • • • • • • • • • •	•••••
				• • • • • • • • • • • • • • • • • • • •		• • • • • • • • • • • • • • • • • • • •				
								•••••		
•••••	•••••	• • • • • • • • • • • • • • • • • • • •	•••••	• • • • • • • • • • • • • • • • • • • •	• • • • • • • • • • • • • • • • • • • •	• • • • • • • • • • • • • • • • • • • •	• • • • • • • • • • • • • • • • • • • •	•••••	• • • • • • • • • • • • • • • • • • • •	• • • • • • • • • • • • • • • • • • • •
• • • • • • • • • • • • • • • • • • • •	•••••	• • • • • • • • • • • • • • • • • • • •	•••••	• • • • • • • • • • • • • • • • • • • •	• • • • • • • • • • • • • • • • • • • •	• • • • • • • • • • • • • • • • • • • •	• • • • • • • • • • • • • • • • • • • •	•••••	• • • • • • • • • • • • • • • • • • • •	• • • • • • • • • • • • • • • • • • • •
				• • • • • • • • • • • • • • • • • • • •		• • • • • • • • • • • • • • • • • • • •				
								•••••		

Please turn over

Explain the functions of both the transistors and the capacitors in this flasher circuit.

4

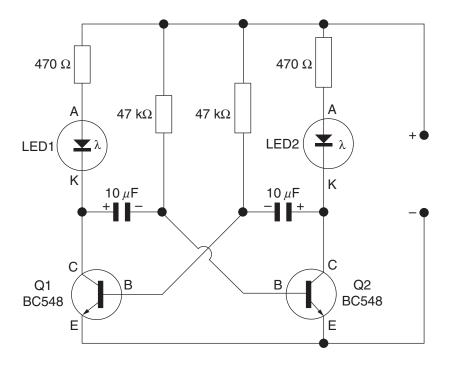

•••••	• • • • • • • • • • • • • • • • • • • •	 	•••••	• • • • • • • • • • • • • • • • • • • •
• • • • • • • • • • • • • • • • • • • •		 	• • • • • • • • • • • • • • • • • • • •	
		 	•••••	• • • • • • • • • • • • • • • • • • • •
•••••	• • • • • • • • • • • • • • • • • • • •	 	• • • • • • • • • • • • • • • • • • • •	

Industrial Technology Electronics Technologies

Section III

15 marks Attempt Question 16 Allow about 35 minutes for this section

Answer the question in a writing booklet provided. Extra writing booklets are available.

Question 16 (15 marks)

- (a) Explain why a company should comply with safety standards. 6
- (b) Assess strategies that a company could implement to establish and maintain a safe work culture.

End of paper

2432 - 13 -