

Question 19 (3 marks)

Name the components of the builder's temporary power supply shown in the diagram.

3

